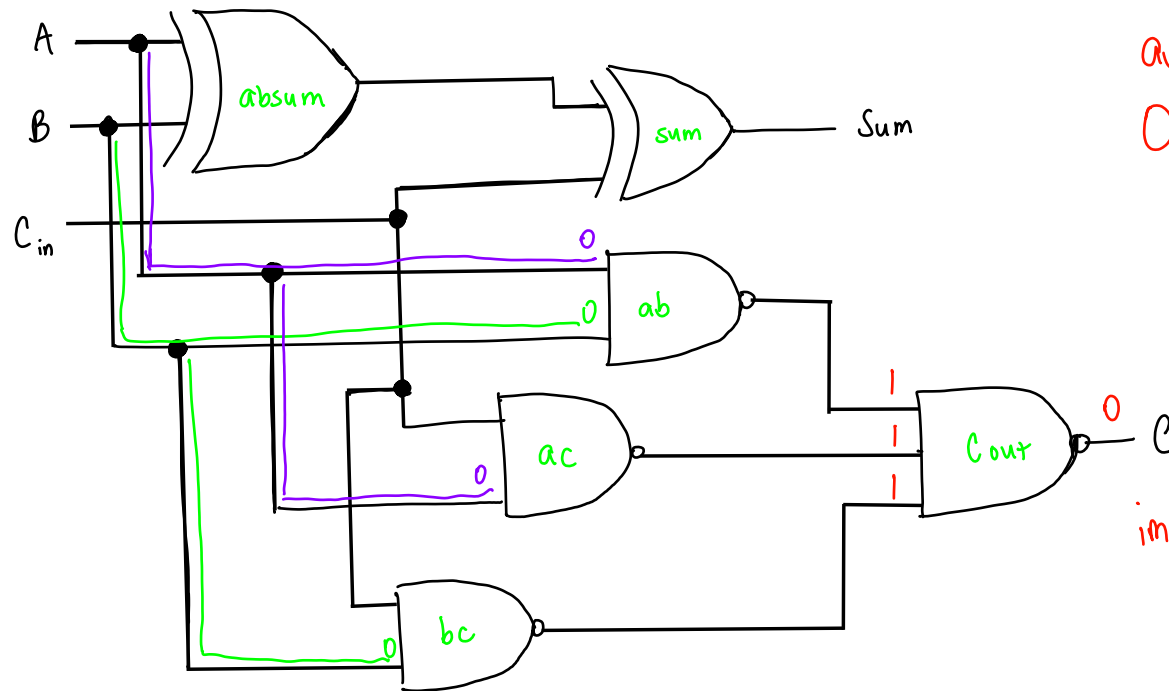


CASES BASED ON INPUT

CASE: 000

as long as there is at least one
0 input, output of nand is 1




immediate 0, w/o counting
for carry

This also applies to CASE: 001



whether carryin is 0 or 1,
it does not matter.

Carry out will remain 0.

automatic and no delay.

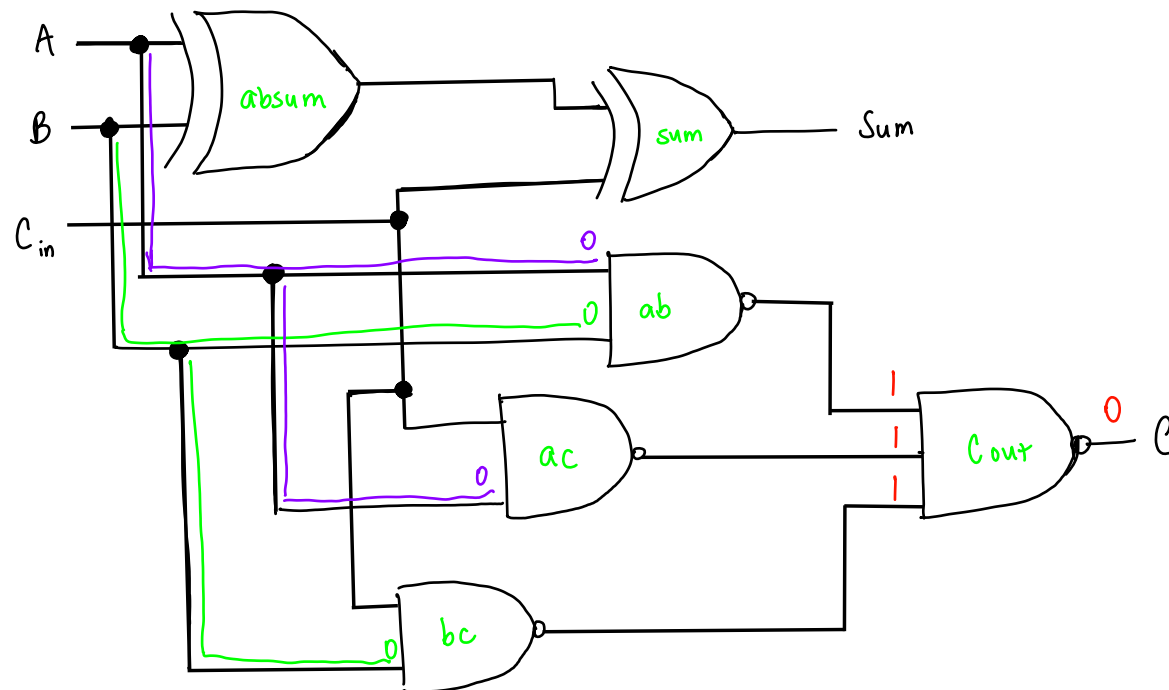


CASE 110 and 111

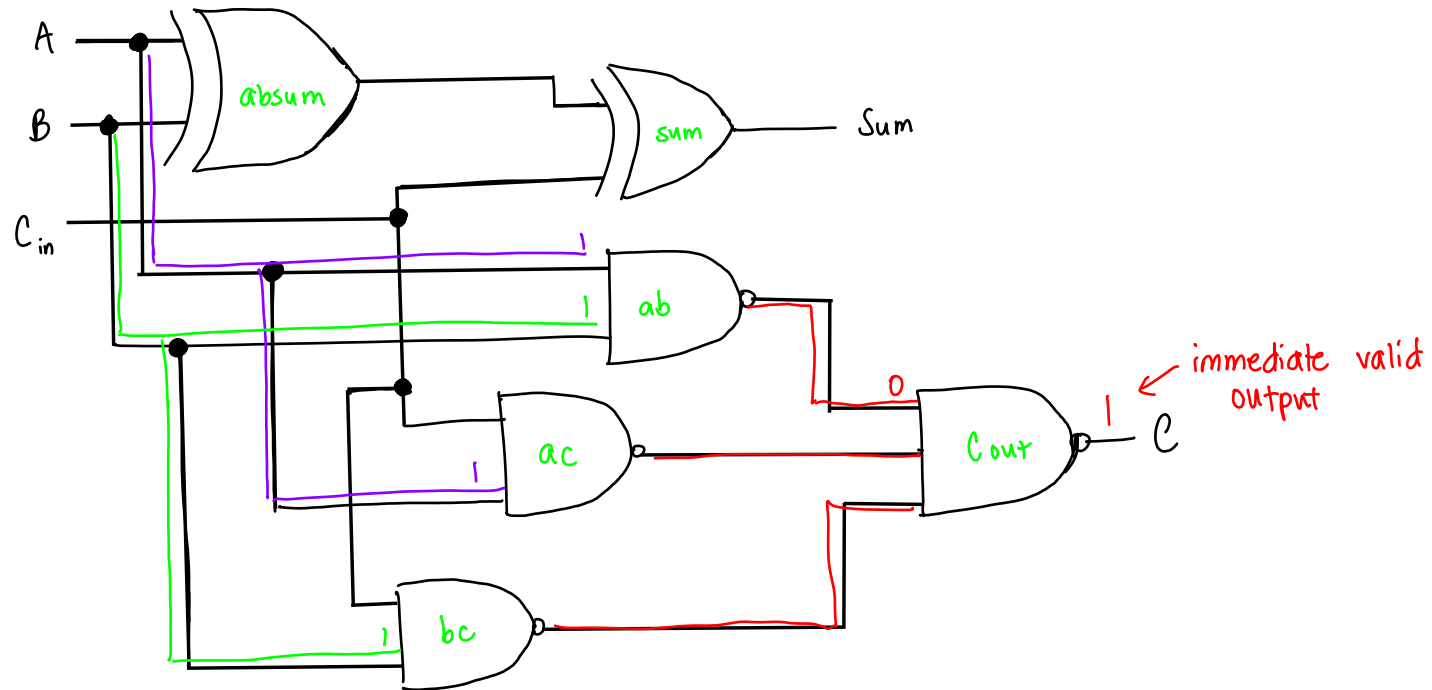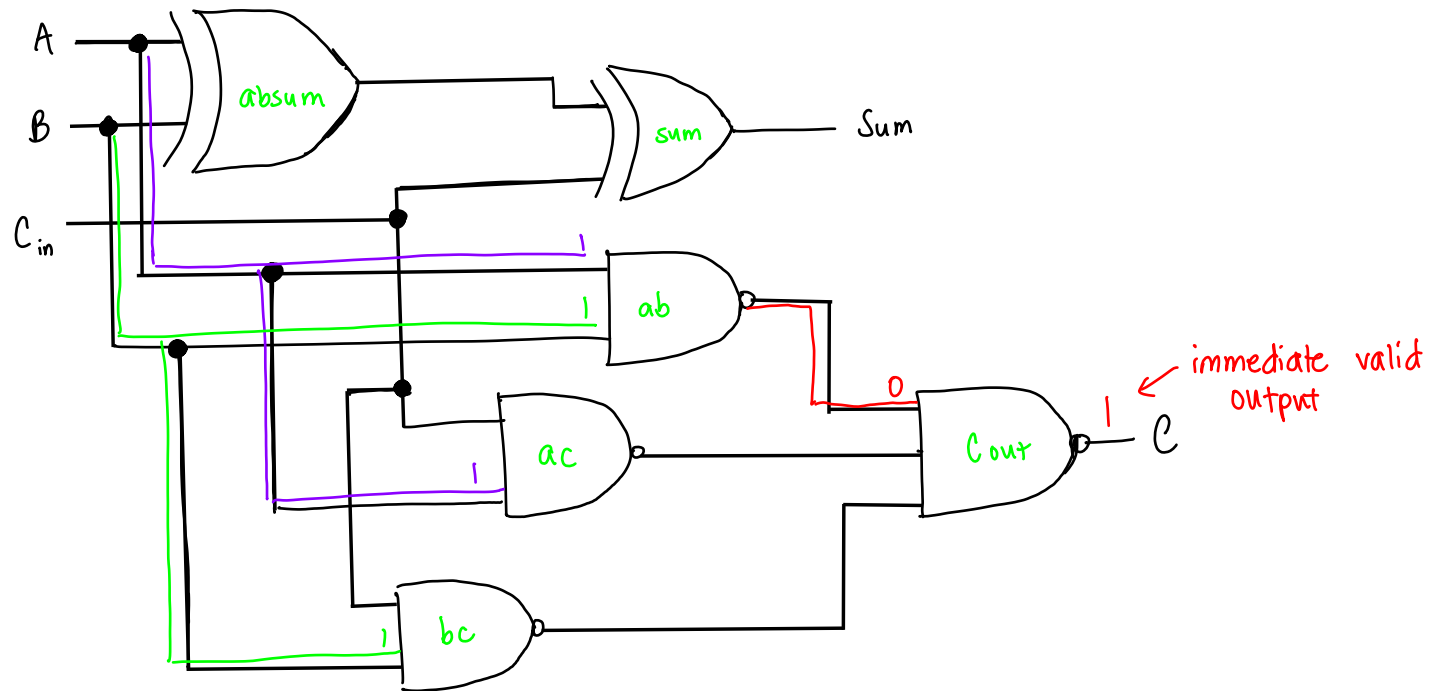


CASE 010 and 100

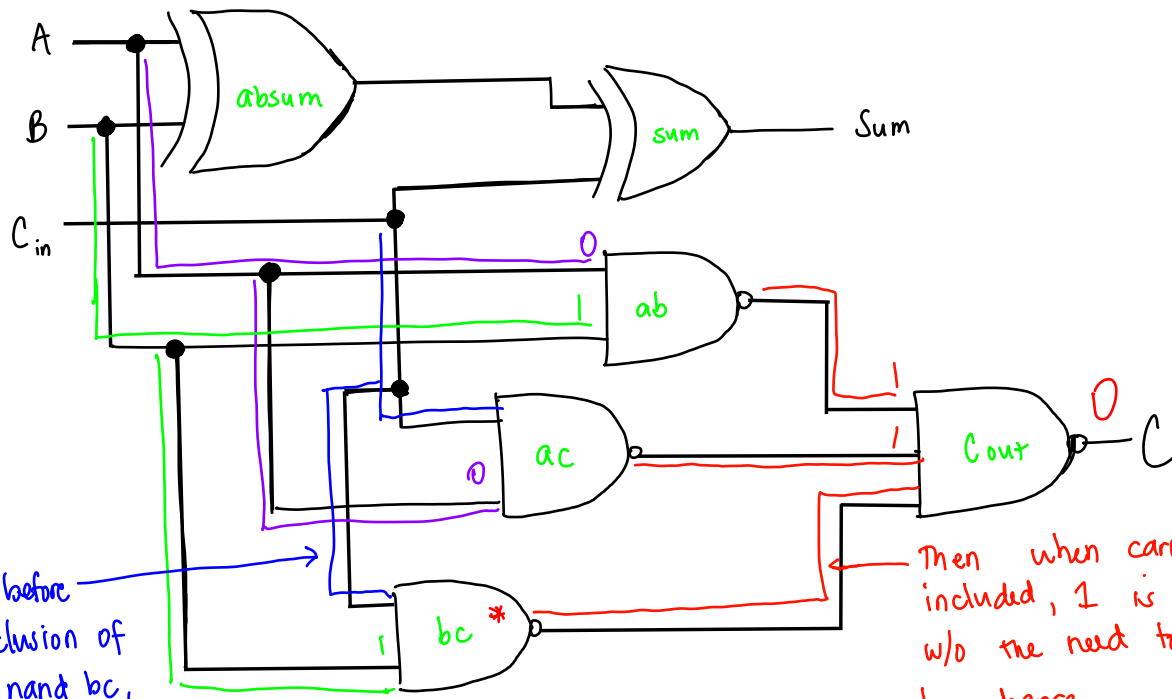(working under the assumption of a "phantom 1", or that the natural state of a nand is 1)




Then when carry in is finally included, 1 is the valid output w/o the need to "trigger" bc nand gate to change.

However, there is still a bit of delay, including the "trigger" for Cout nand.

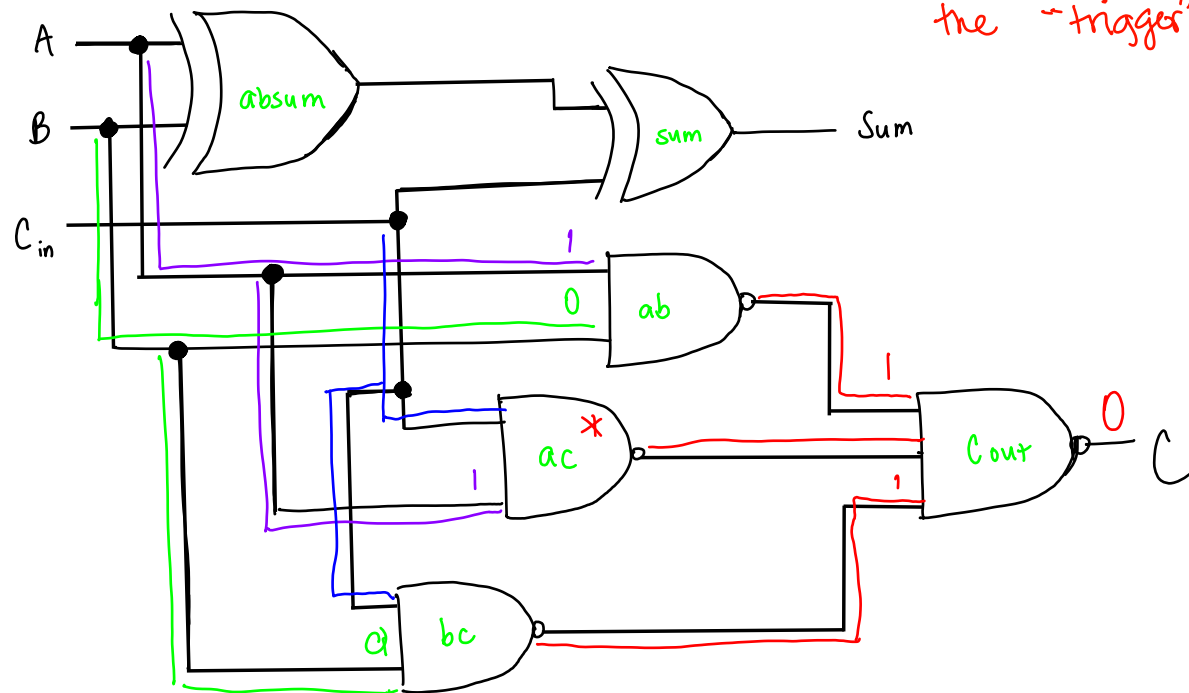


CASE 011

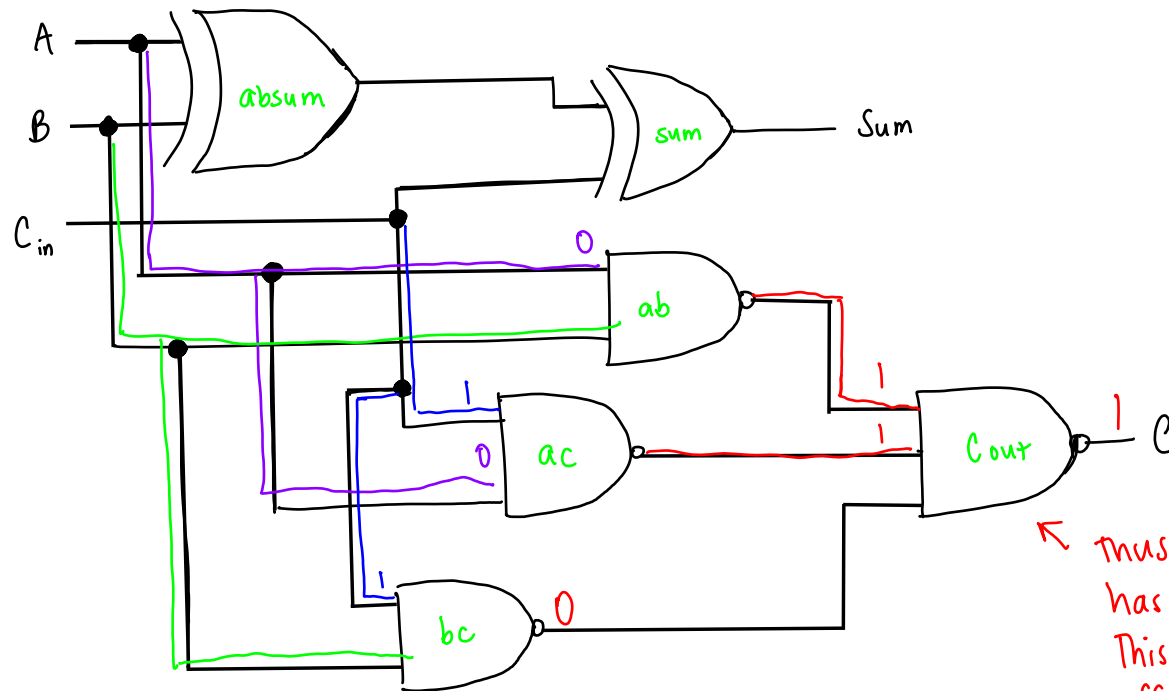


needs carry in and needs to be "triggered" from 1 to 0

thus, C_{out} depends or has to wait for nand bc. This delay will have the ripple adder effect

CASE 101

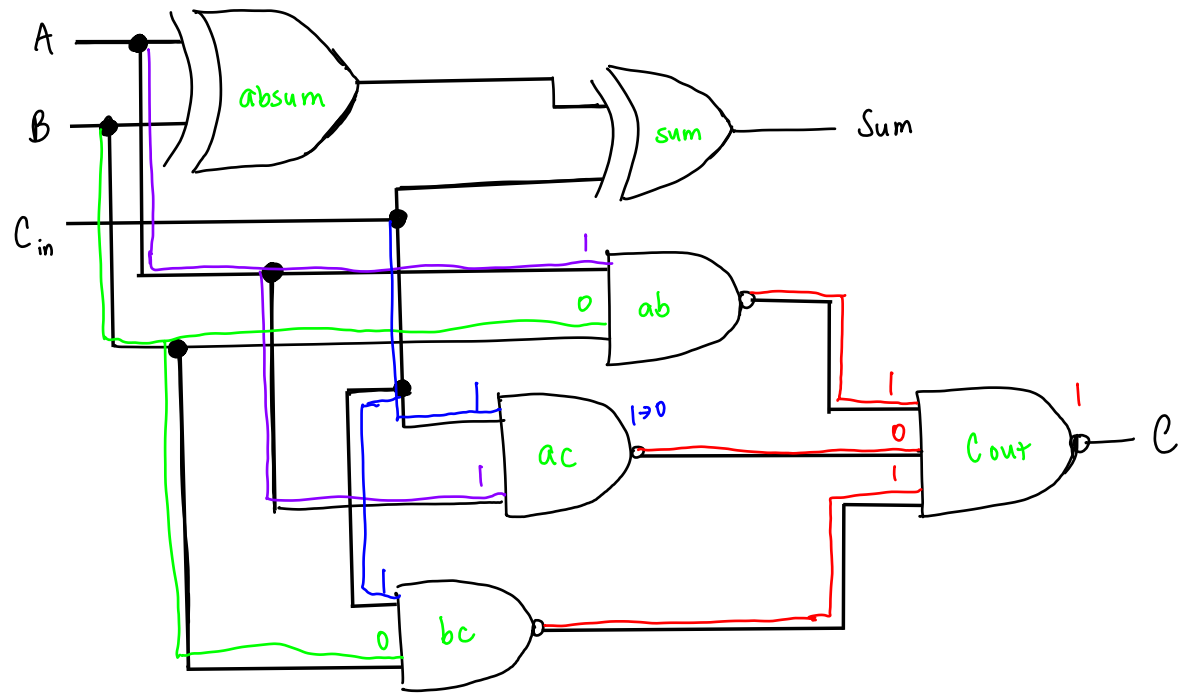

 

Parallel Adder \rightarrow the addition of all bits is happening parallelly; FAs are connected parallelly

\hookrightarrow Assumption: application of input bits \Rightarrow immediate availability of all sum bit and carry bit at the output.

Reality: valid output is actually available AFTER CERTAIN DELAY

Delay depends on the propagation delays of the internal circuit of that block and the individual logic gates.

\downarrow
 \leftarrow PROPAGATION DELAY = t_p (ns \rightarrow ms)
 - amount of time for output (in this case) to be valid
 (CSC151.01)