

JSim Quick Reference v0.1

Iterators

	Syntax	Effect
duplication	A#5	A A A A A
buses	A[4:0]	A4 A3 A2 A1 A0
	A[11:10]	A11 A10
	A1[1:0] // DANGER!	A11 A10 // DANGER! Same as above!
	A1_[1:0] // SAFE	A1_1 A1_0
	A[1:0]#2	A1 A0 A1 A0
	A[7:0:2]	A7 A5 A3 A1
	A[2:0][1:0]	A21 A20 A11 A10 A01 A00
subcircuits	Xfoo A[2:0] B[1:0] Q Z[2:0] and2	Xfoo#0 A2 B1 Z2 and2 Xfoo#1 A1 B0 Z1 and2 Xfoo#2 A0 Q Z0 and2
connect (WRONG)	.connect A[1:0] B[1:0] // WRONG	.connect A1 A0 // Probably not .connect A1 B1 // what you .connect A1 B0 // wanted
connect (RIGHT)	.subckt S T join .connect S T .ends XjAB A[1:0] B[1:0] join	.connect A1 B1 .connect A0 B0 // Much better!

Device Statements

Subcircuit	Xid nodes... subname
Capacitor	Cid n+ n- capacitance
Inductor	Lid n+ n- inductance
Resistor	Rid n+ n- resistance
Current Source	Iid n+ n- {{DC=}dcvalue} {tran}
Voltage Source	Vid n+ n- {{DC=}dcvalue} {tran}
	// tran options:
	pulse(vA,vB,tdelay,tAtoB,tBtoA,tstable) // for clocks, starts at vA for tdelay, period is 2*tstable + tAtoB + tBtoA
	pwl(t1 v1, t2 v2, t3 v3 ...) // for reset signals, signal transitions linearly from v1 at t1 to v2 at t2
MOSFET	Mid ndrain ngate nsource nbulk model L=meters W=meters {params} // a MOSFET exactly specified by L and W
MOSFET (Scaled)	Mid ndrain ngate nsource nbulk model SL=integer SW=integer {params} // a MOSFET specified by SL*SCALE and SW*SCALE // requires the .option SCALE=meters statement, defined in nominal.jsim
	// model is NENH or PENH, defined in stdcell.jsim
VCVS	Eid n+ n- ctl+ ctl- gain // voltage-controlled voltage source
CCCS	Fid n+ n- ctl+ ctl- gain // current-controlled current source
VCCS	Gid n+ n- ctl+ ctl- gain // voltage-controlled current source
CCVS	Hid n+ n- ctl+ ctl- gain // current-controlled voltage source
Digital Waveform	Wid nodes... nrz(vlow,vhigh,tperiod,tdelay,trise,tfall) data...
Memory	Xid ports... \$memory width=w nlocations=nloc options... // each port has: oe clk wen a _{naddr-1} ... a ₀ d _{w-1} ... d ₀ // option file="filename" path is relative to jsim.jar location

Control Statements

.connect	.connect nodes... // connect all nodes together	
.dc	.dc Vds 0 5 .1 Vgs 0 5 1 // dc analysis with voltage supplies // sweep Vds 0-5V in 0.1V steps // one plot each for Vgs 0-5V in 1V steps	
.global	.global vdd // node vdd is now accessible when creating subcircuits	
.include	.include "filename" // the contents of filename are included in the current file // path is relative to the including file	
.option	.option SCALE=35nm // set value of option SCALE to 35nm	
.plot	.plot A .plot b(B[3:0]) .plot d(...) .plot I(Vid) .plot L(...) .plot o(...) .plot sd(...) .plot x(...)	analog signal or bus format a bus as unsigned binary format a bus as unsigned decimal current into n+ of a voltage source format a bus as unsigned hexadecimal format a bus as unsigned octal format a bus as signed decimal format a bus as unsigned hexadecimal, same as L()
.plotdef	.plotdef Snakes Cobra Mamba Copperhead Sidewinder // when used with .plot Snakes(A[1:0]), displays snake names // zero value name first, case sensitive	
.subckt	.subckt subname nodes... .ends // create a subcircuit named subname	
.temp	.temp 100 // set circuit temperature to 100C	
.tran	.tran 100us // transient simulation for 100us	

Numbers

All jsim numbers are in SI units: meters, Farads, Henries, Volts, etc. Take care not to declare capacitors that are 8 meters wide.

A number may be an integer (12, -44), a floating point number (3.14159), an integer or floating point number followed by an integer exponent (1E-14, 2.65E3), or an integer or a floating point number followed by a scale factor.

Letters immediately following a number that are not scale factors are ignored and letters immediately following a scale factor are ignored. Integers can be entered in binary, octal or hexadecimal notation by using the appropriate prefix:

0b1011101110100	6004 in binary ("0b" prefix)
013564	6004 in octal ("0" prefix)
0x1774	6004 in hex ("0x" prefix)

Scale Factor	Pronounced	Multiplier
T, t	tera	1E12
G, g	giga	1E9
MEG, meg	mega	1E6
K, k	kilo	1E3
M, m	milli	1E-3
U, u	micro	1E-6
MIL, mil		25.4E-6
N, n	nano	1E-9
P, p	pico	1E-12
F, f	femto	1E-15

Useful Advice

- "0" is ground.
- Don't end bus names with numbers. See above.
- Ctrl+S doesn't save, you must use the save button.
- You can add plots after you simulate, just type a plot command in the white boxes.
- Plot "0", it will be easier to see the time on a plot of "0".

Standard Cell Library from nominal.jsim

<i>Netlist</i>	<i>Function</i>	t_{CD} (ns)	t_{PD} (ns)	t_R (ns/pf)	t_F (ns/pf)	<i>load</i> (pf)	<i>size</i> (μ^2)
Xid z constant0	$Z = 0$	—	—	—	—	—	0
Xid z constant1	$Z = 1$	—	—	—	—	—	0
Xid a z inverter	$Z = \overline{A}$.005	.02	2.3	1.2	.007	10
Xid a z inverter_2		.009	.02	1.1	.6	.013	13
Xid a z inverter_4		.009	.02	.56	.3	.027	20
Xid a z inverter_8		.02	.11	.28	.15	.009	56
Xid a z buffer	$Z = A$.02	.08	2.2	1.2	.003	13
Xid a z buffer_2		.02	.07	1.1	.6	.005	17
Xid a z buffer_4		.02	.07	.56	.3	.01	30
Xid a z buffer-8		.02	.07	.28	.15	.02	43
Xid e a z tristate	$Z = A$ when e=1 else Z not driven	.03	.15	2.3	1.3	.004	23
Xid e a z tristate_2		.03	.13	1.1	.6	.006	30
Xid e a z tristate_4		.02	.12	.6	.3	.011	40
Xid e a z tristate_8		.02	.11	.3	.17	.02	56
Xid a b z and2	$Z = A \cdot B$.03	.12	4.5	2.3	.002	13
Xid a b c z and3	$Z = A \cdot B \cdot C$.03	.15	4.5	2.6	.002	17
Xid a b c d z and4	$Z = A \cdot B \cdot C \cdot D$.03	.16	4.5	2.5	.002	20
Xid a b z nand2	$Z = \overline{A \cdot B}$.01	.03	4.5	2.8	.004	10
Xid a b c z nand3	$Z = \overline{A \cdot B \cdot C}$.01	.05	4.2	3.0	.005	13
Xid a b c d z nand4	$Z = \overline{A \cdot B \cdot C \cdot D}$.01	.07	4.4	3.5	.005	17
Xid a b z or2	$Z = A + B$.03	.15	4.5	2.5	.002	13
Xid a b c z or3	$Z = A + B + C$.04	.21	4.5	2.5	.003	17
Xid a b c d z or4	$Z = A + B + C + D$.06	.29	4.5	2.6	.003	20
Xid a b z nor2	$Z = \overline{A + B}$.01	.05	6.7	2.4	.004	10
Xid a b c z nor3	$Z = \overline{A + B + C}$.02	.08	8.5	2.4	.005	13
Xid a b c d z nor4	$Z = \overline{A + B + C + D}$.02	.12	9.5	2.4	.005	20
Xid a b z xor2	$Z = A \oplus B$.03	.14	4.5	2.5	.006	27
Xid a b z xnor2	$Z = \overline{A \oplus B}$.03	.14	4.5	2.5	.006	27
Xid a1 a2 b z aoiz21	$Z = \overline{(A1 \cdot A2) + B}$.02	.07	6.8	2.7	.005	13
Xid a1 a2 b z oai21	$Z = \overline{(A1 + A2) \cdot B}$.02	.07	6.7	2.7	.005	17
Xid s d0 d1 z mux2	$Z = D0$ when $S = 0$ $Z = D1$ when $S = 1$.02	.12	4.5	2.5	.005	27
Xid s0 s1 d0 d1 d2 d3 z mux4 (Note order of s0 and s1!)	$Z = D0$ when $S_0 = 0, S_1 = 0$ $Z = D1$ when $S_0 = 1, S_1 = 0$ $Z = D2$ when $S_0 = 0, S_1 = 1$ $Z = D3$ when $S_0 = 1, S_1 = 1$.04	.19	4.5	2.5	.006	66
Xid d clk q dreg $t_{\text{setup}} = .15, t_{\text{hold}} = 0$	$D \rightarrow Q$ on $\text{CLK} \uparrow$.03	.19	4.3	2.5	.002	56
Xid d clk q dlatch (do not use)	$D \rightarrow Q$ while $\text{CLK} \uparrow$.03	.19	4.3	2.5	.002	36